

# CSU22022 Computer Architecture

Michael Manzke

## Project 2

### MICROCODED INSTRUCTION SET PROCESSOR

30 November 2020

#### Description:

The second project will implement a Microprogrammed Instruction Set Processor. This builds on the VHDL model from the first project.

The following modifications are required:

- Increase the number of registers in the register-file from 32 to 33.
- This requires an additional select bit for the two multiplexers (Bus A and Bus B) and the destination decoder. These are separate signals (TD, TA, TB) from the Control Memory. See Figure 1. The size of the registers in the register-file is 32 bits.
- Consequently all components of the Datapath (e.g. MUXs in the register-file, decoder in the Register file, Arithmetic/logic Unit, Shifter and MUXs) are 32 bit operations.
- Add and test Memory M (512 x 32) and Control Memory (256 x 41) to your project. MUX M will feed 32 bit addresses from either the Bus A or the PC into the Memory M but only the 9 least significant address bits will be used to index into the array. This restricts the memory size to 512. Furthermore, the CAR feeds 17 bit addresses into the the Control Memory but only the 8 least significant address will be used to select a memory location in the Control Memory.
- Implement all the components shown in Figure 1 on page 3.
- Design reset logic for PC and CAR registers. This will enable you to start your program.
- Write microprogramms for the Control Memory that implement the following instructions:
  - ADI, LD, SR, INC, NOT, ADD, unconditional jump, and conditional branch (only one condition).

- Write machine code for the Memory M that demonstrates the use of the following instructions:
  - ADI, LD, SR, INC, NOT, ADD, unconditional jump, and conditional branch (only one condition).

Table 1: FS code definition

FS	MF Select	G Select	H Select	Micro-operation
00000	0	0000	00	$F = A$
00001	0	0001	00	$F = A + 1$
00010	0	0010	00	$F = A + B$
00011	0	0011	00	$F = A + B + 1$
00100	0	0100	01	$F = A + \bar{B}$
00101	0	0101	01	$F = A + \bar{B} + 1$
00110	0	0110	01	$F = A - 1$
00111	0	0111	01	$F = A$
01000	0	1000	00	$F = A \wedge B$
01010	0	1010	10	$F = A \vee B$
01100	0	1100	10	$F = A \oplus B$
01110	0	1110	10	$F = \bar{A}$
10000	1	0000	00	$F = B$
10100	1	0100	01	$F = srB$
11000	1	1000	10	$F = slB$

The Microprogrammed Instruction Set Processor block diagram is shown in Figure 1 on page 3. Figure 1 is based on Figure 8-26 in Mano and Kime [2] but was modified to suit the assignment.

The Functional Unit should have the functionality defined in the Table 1 on page 2.

Discuss your simulation results. The CSU22022 lecture notes provide the necessary information to complete the project.

If the entire project is working (you must demonstrate that you can execute the following instructions: ADI, LD, SR, INC, NOT, ADD, unconditional jump, and conditional branch (only one condition)), you can gain additional 20% by implementing a carry-lookahead adder (CLA).

**DUE: Tuesday, 5<sup>th</sup> January 2021**

Please submit your VHDL-code and test-benches including all simulation results to Blackboard.



#### References:

- [1] J Morris Mano and Charles R. Kime. Logic and computer design fundamentals.
- [2] M. Morris Mano and Charles R. Kime. Logic and Computer Design Fundamentals: chapter 7. Prentice Hall, 2nd edition updated edition, 2001.